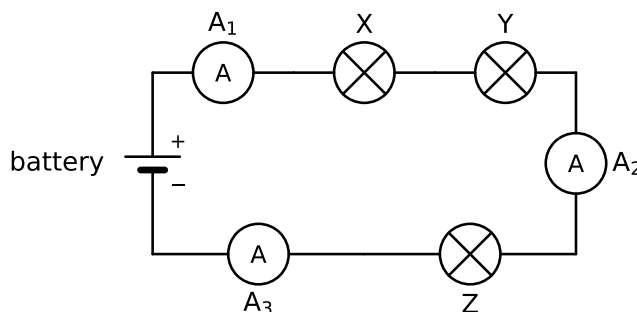


Part A: Concepts

1. Three identical bulbs X, Y, and Z are connected in series with a battery and three ammeters.




- Ammeter A_1 reads 0.50 A. What do A_2 and A_3 read? Explain.
- Bulb Y burns out. What happens to bulbs X and Z? Explain.
- A fourth identical bulb is added in series. What happens to the total resistance, the current, and the brightness of each bulb?
 - Both read **0.50 A**. There is only one path, and charge is not used up, so the current is the same everywhere in a series circuit.
 - X and Z **go out**. The broken filament opens the only loop, so the current stops everywhere.
 - The total resistance **increases** (resistances add), so the current **decreases**, and every bulb gets **dimmer**.

Part B: Solving Series Circuits

Show your equations, substitutions, and answers with units.

2. A 12 V battery is connected in series with three resistors: 4.0 Ω , 8.0 Ω , and 12 Ω .
- Find the total resistance.
 - Find the current through each resistor.
 - Find the voltage drop across each resistor, and check that the drops add to 12 V.
 - Which resistor has the biggest voltage drop? Why does that make sense?
 - $R_T = 4.0 \Omega + 8.0 \Omega + 12 \Omega = \mathbf{24 \Omega}$
 - $I = V/R_T = 12 \text{ V} / 24 \Omega = \mathbf{0.50 \text{ A}}$, the same through every resistor
 - $V_1 = (0.50 \text{ A})(4.0 \Omega) = \mathbf{2.0 \text{ V}}$, $V_2 = (0.50 \text{ A})(8.0 \Omega) = \mathbf{4.0 \text{ V}}$, $V_3 = (0.50 \text{ A})(12 \Omega) = \mathbf{6.0 \text{ V}}$. Check: $2.0 \text{ V} + 4.0 \text{ V} + 6.0 \text{ V} = 12 \text{ V}$.
 - The **12 Ω** resistor. Every resistor has the same current, so by $V = IR$ the biggest resistance gets the biggest share of the voltage.

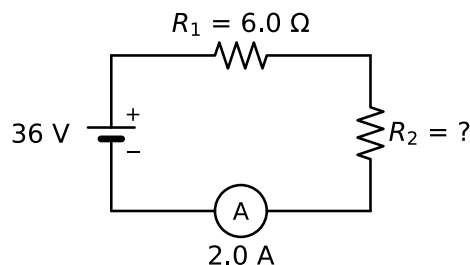3. Find the total resistance, the unknown resistance R_2 , and the voltage drop across each resistor.




Total resistance: $R_T = V/I = 36 \text{ V} / 2.0 \text{ A} = \mathbf{18 \Omega}$

Unknown: $R_2 = R_T - R_1 = 18 \Omega - 6.0 \Omega = \mathbf{12 \Omega}$

Drops: $V_1 = (2.0 \text{ A})(6.0 \Omega) = \mathbf{12 \text{ V}}$, $V_2 = (2.0 \text{ A})(12 \Omega) = \mathbf{24 \text{ V}}$. Check: $12 \text{ V} + 24 \text{ V} = 36 \text{ V}$.

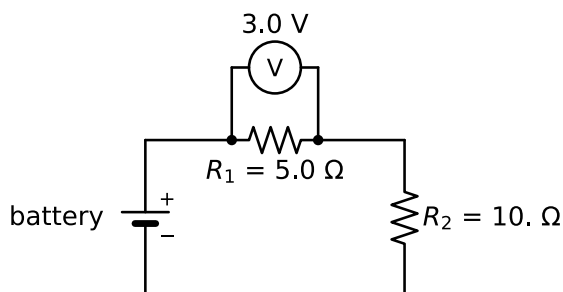4. A voltmeter across R_1 reads 3.0 V. Find the current in the circuit, the voltage across R_2 , and the battery voltage.



Current: $I = V_1/R_1 = 3.0 \text{ V} / 5.0 \Omega = \mathbf{0.60 \text{ A}}$ (the same everywhere)

Across R_2 : $V_2 = IR_2 = (0.60 \text{ A})(10. \Omega) = \mathbf{6.0 \text{ V}}$

Battery: $V = V_1 + V_2 = 3.0 \text{ V} + 6.0 \text{ V} = \mathbf{9.0 \text{ V}}$. (Or $V = IR_T = (0.60 \text{ A})(15 \Omega) = 9.0 \text{ V}$.)

5. An old string of holiday lights has 40 identical 6.0Ω bulbs connected in series to a 120 V outlet.
- What is the current in the string?
 - What is the voltage across each bulb?
 - What is the power of each bulb?
 - One bulb burns out. How many bulbs stay lit? Explain.
- a.** $R_T = 40 \times 6.0 \Omega = 240 \Omega$, so $I = 120 \text{ V} / 240 \Omega = \mathbf{0.50 \text{ A}}$
- b.** $V = IR = (0.50 \text{ A})(6.0 \Omega) = \mathbf{3.0 \text{ V}}$ (also $120 \text{ V} / 40 \text{ bulbs} = 3.0 \text{ V}$)
- c.** $P = I^2R = (0.50 \text{ A})^2(6.0 \Omega) = \mathbf{1.5 \text{ W}}$ (or $P = IV = (0.50 \text{ A})(3.0 \text{ V}) = 1.5 \text{ W}$)
- d. None.** The burned-out bulb opens the only loop, so the current stops and all 40 bulbs go dark.