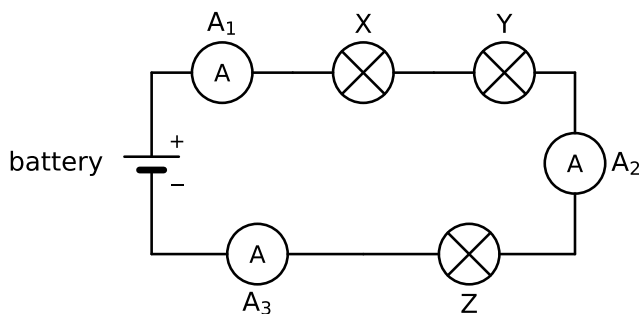


Part A: Concepts

1. Three identical bulbs X, Y, and Z are connected in series with a battery and three ammeters.




- a. Ammeter A_1 reads 0.50 A. What do A_2 and A_3 read? Explain.
- b. Bulb Y burns out. What happens to bulbs X and Z? Explain.
- c. A fourth identical bulb is added in series. What happens to the total resistance, the current, and the brightness of each bulb?

Part B: Solving Series Circuits


Show your equations, substitutions, and answers with units.

2. A 12 V battery is connected in series with three resistors: 4.0 Ω , 8.0 Ω , and 12 Ω .
- Find the total resistance.
 - Find the current through each resistor.
 - Find the voltage drop across each resistor, and check that the drops add to 12 V.
 - Which resistor has the biggest voltage drop? Why does that make sense?

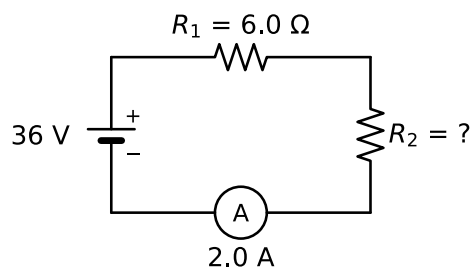3. Find the total resistance, the unknown resistance R_2 , and the voltage drop across each resistor.



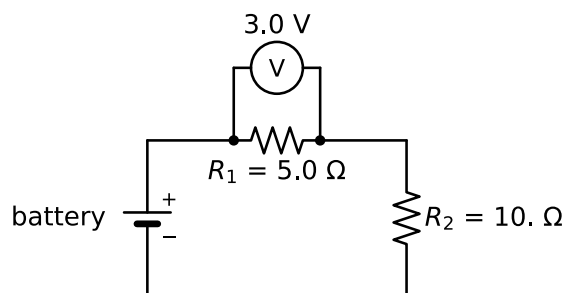-
4. A voltmeter across R_1 reads 3.0 V. Find the current in the circuit, the voltage across R_2 , and the battery voltage.



-
5. An old string of holiday lights has 40 identical $6.0 \, \Omega$ bulbs connected in series to a 120 V outlet.
- What is the current in the string?
 - What is the voltage across each bulb?
 - What is the power of each bulb?
 - One bulb burns out. How many bulbs stay lit? Explain.